

**EECE 2160 – Embedded Design, Enabling Robotics**

## Homework #2


Assigned: Monday, Sept. 23, 2024. Due: Monday, Sept. 30 at 11:59pm on Canvas

5 Problems, 100 points Total

**Problem 1.** (20 points)

Redraw this circuit using only 2-input NAND gates. Draw neatly!!

See Lecture 3 slides 41 to 45.

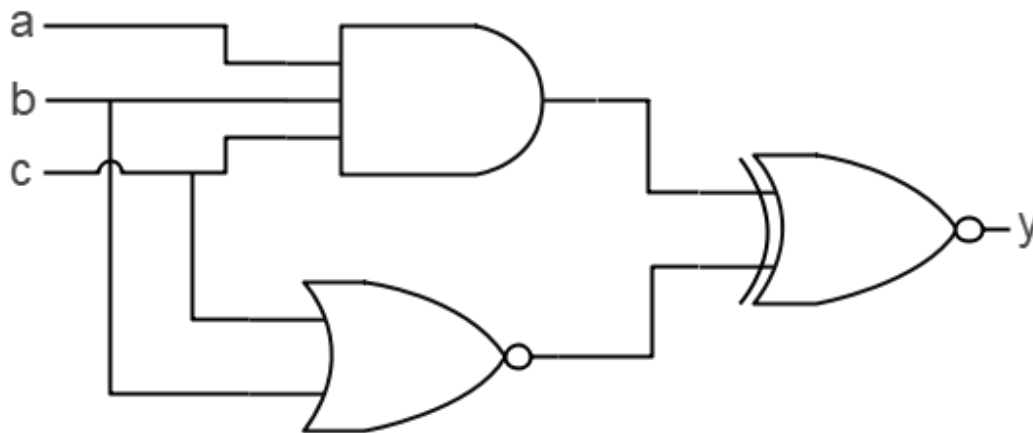

**Problem 2.** (20 points total, 5 points each)

Consider the following Truth Table:


Inputs			Output
A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- (5 points) Write the Boolean equation for this truth table in Sum of Products form.
- (10 points) Minimize the Boolean equation using the axiom and theorems of Boolean Algebra. State the theorems and axioms used.
- (5 points) Draw the digital circuit from the simplified equation.

**Problem 3.** (20 points total)

Write the Boolean equations (note plural) for the circuit shown below. No need to simplify.

Hint: Think Sum of Products.

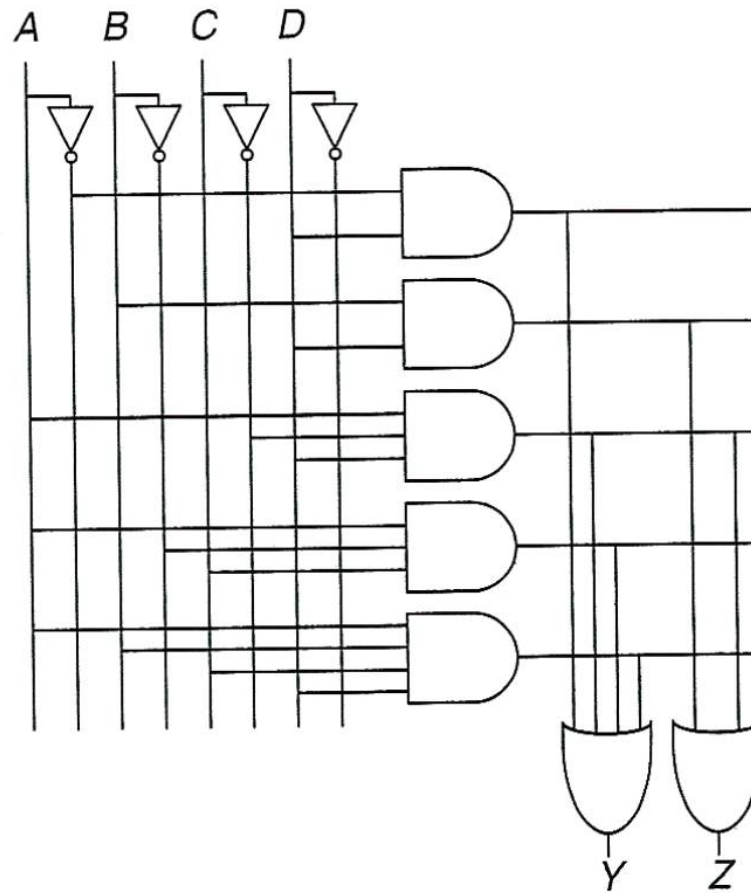

**Problem 4.** (30 points)


Consider this truth table:

Inputs			Output
X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

- (5 points) Write the Boolean equation from the truth table using the sum of products method.
- (10 points) Simplify the equation using the Theorems and Axioms of Boolean algebra. State the theorems and axioms used.
- (10 points) Write the Boolean equation from the truth table using a **Karnaugh map**.
- (5 points) Do the equations from parts b and c agree? If not, then can you transform one of the equations into the other?

**Problem 5.** (10 points total, 5 points each)

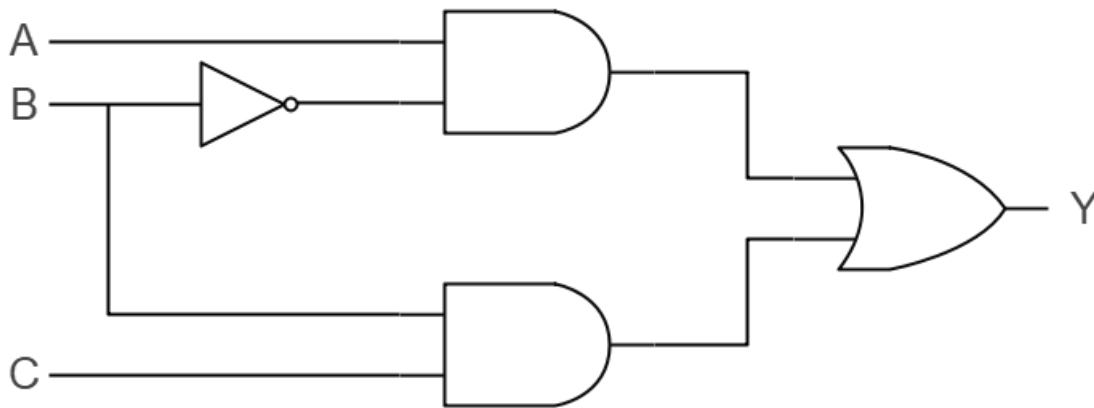- a. Write the Boolean equation for the circuit shown below. No need to simplify.



- b. Rename the inputs and outputs as follows:

A = D0

C = D1

B = Select

Y = Out

What is the name of this circuit? It is a widely used combinational circuit (see Lecture 6).