

# EECE 2160 – Embedded Design, Enabling Robotics

## Homework #2


Assigned: Monday, Sept. 23, 2024. Due: Monday, Sept. 30 at 11:59pm on Canvas

5 Problems, 100 points Total


### Problem 1. (20 points)

Redraw this circuit using only 2-input NAND gates. Draw neatly!!

See Lecture 3 slides 41 to 45.

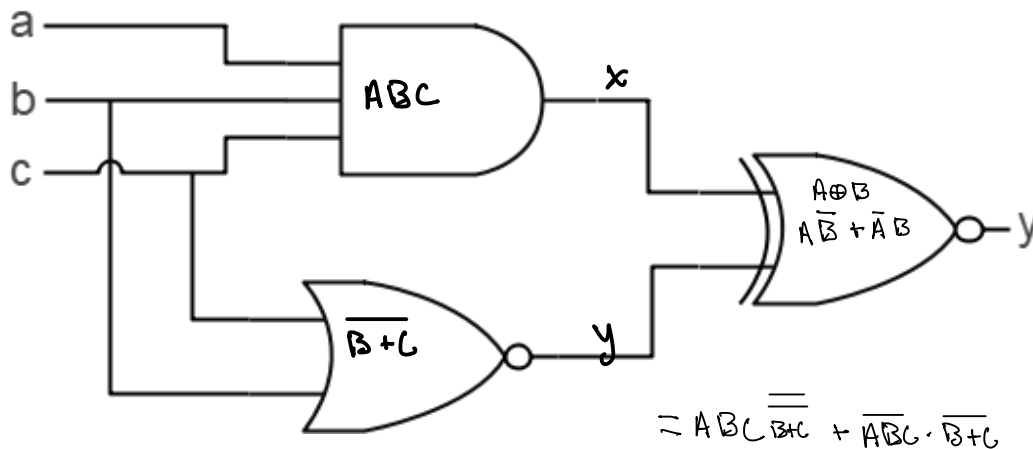
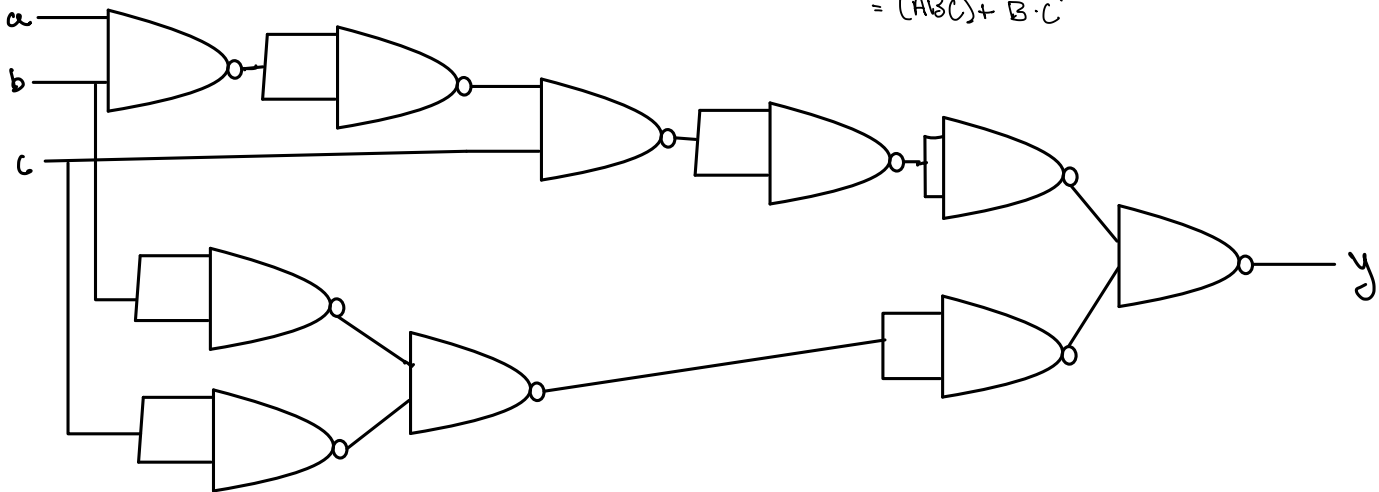
$$\begin{aligned} &= ABC + \overline{B+C} \\ &= ABC + \overline{B} \cdot \overline{C} \end{aligned}$$



$$\overline{(\overline{AB} \cdot \overline{AB}) \cdot C} \cdot \overline{(\overline{AB} \cdot \overline{AB}) \cdot C} \cdot \overline{(\overline{AB} \cdot \overline{AB}) \cdot C} \cdot \overline{(\overline{AB} \cdot \overline{AB}) \cdot C} \cdot \overline{(\overline{BB} \cdot \overline{C})} \cdot \overline{(\overline{BB} \cdot \overline{C})}$$

**Problem 2.** (20 points total, 5 points each)

Consider the following Truth Table:

Inputs			Output
A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 $\overline{A}BC$  $AB\overline{C}$  $ABC$ 

- (5 points) Write the Boolean equation for this truth table in Sum of Products form.
- (10 points) Minimize the Boolean equation using the axiom and theorems of Boolean Algebra. State the theorems and axioms used.
- (5 points) Draw the digital circuit from the simplified equation.

A.

$$Y = \overline{A}BC + AB\overline{C} + ABC$$

B.

$$Y = \overline{A}BC + AB\overline{C} + ABC$$

$$= (\overline{A} + B)C + AB\overline{C} + ABC$$

de Morgan


$$= (\overline{A} + \overline{B})C + AB(\overline{C} + C)$$

Distributive

$$= (\overline{A} + \overline{B})C + AB$$

Complement


C.

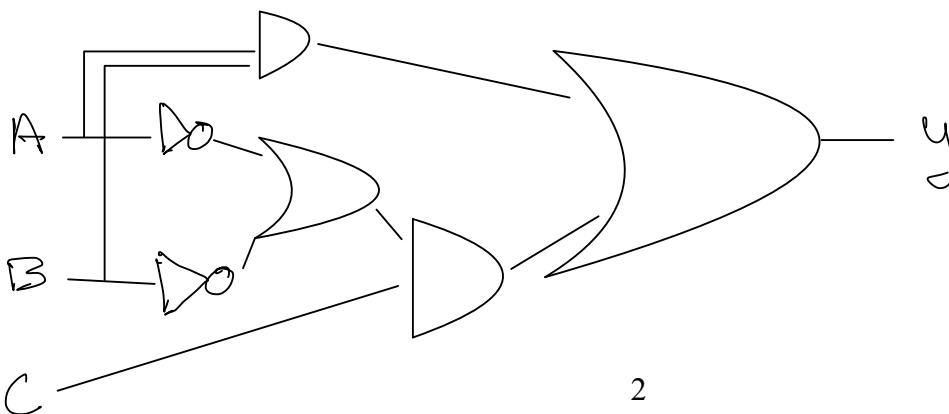

**Problem 3.** (20 points total)

Write the Boolean equations (note plural) for the circuit shown below. No need to simplify.

Hint: Think Sum of Products.

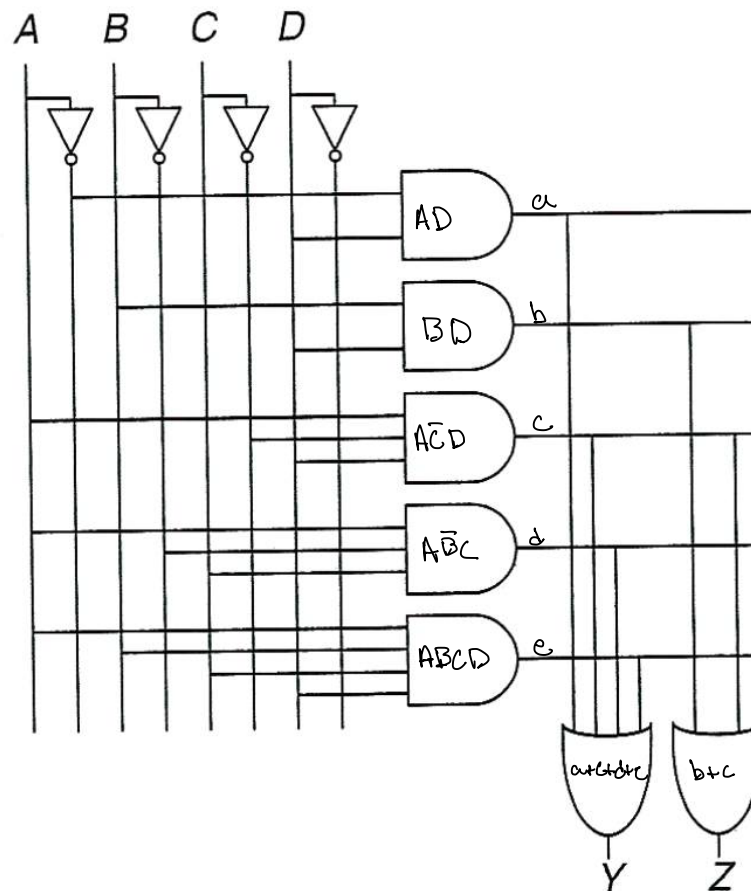

$$Y = a + c + d + e$$

$$= AD + A\bar{C}D + A\bar{B}C + ABC$$

$$Z = b + c$$

$$= BD + A\bar{C}D$$

**Problem 4.** (30 points)

Consider this truth table:

Inputs			Output
X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$\overline{x}yz$

$\overline{x}y\overline{z}$

$x\overline{y}\overline{z}$

$x\overline{y}z$

- (5 points) Write the Boolean equation from the truth table using the sum of products method.
- (10 points) Simplify the equation using the Theorems and Axioms of Boolean algebra. State the theorems and axioms used.
- (10 points) Write the Boolean equation from the truth table using a **Karnaugh map**.
- (5 points) Do the equations from parts b and c agree? If not, then can you transform one of the equations into the other?

$$A. F = \overline{x}yz + \overline{x}y\overline{z} + x\overline{y}\overline{z} + x\overline{y}z$$

$$\begin{aligned}
 B. F &= \overline{x}yz + \overline{x}y\overline{z} + x\overline{y}\overline{z} + x\overline{y}z \\
 &= \overline{y}\overline{z}(\overline{x} + x) + x\overline{y}z && \text{distributive} \\
 &= \overline{y}\overline{z}(1 + x) + x\overline{y}z && \text{Identity} \\
 &= \overline{y}\overline{z} + x\overline{y}z && \text{null element} \\
 &= \overline{y}(\overline{z} + xz) && \text{distribution} \\
 &= \overline{y}(1 + x) && \text{Identity} \\
 &= \overline{y} && \text{null element}
 \end{aligned}$$

C.


		yz			
		00	01	11	10
x	0	1	1	0	0
	1	1	1	0	0

$= \overline{y}$

D. The equations agree. 4

**Problem 5.** (10 points total, 5 points each)

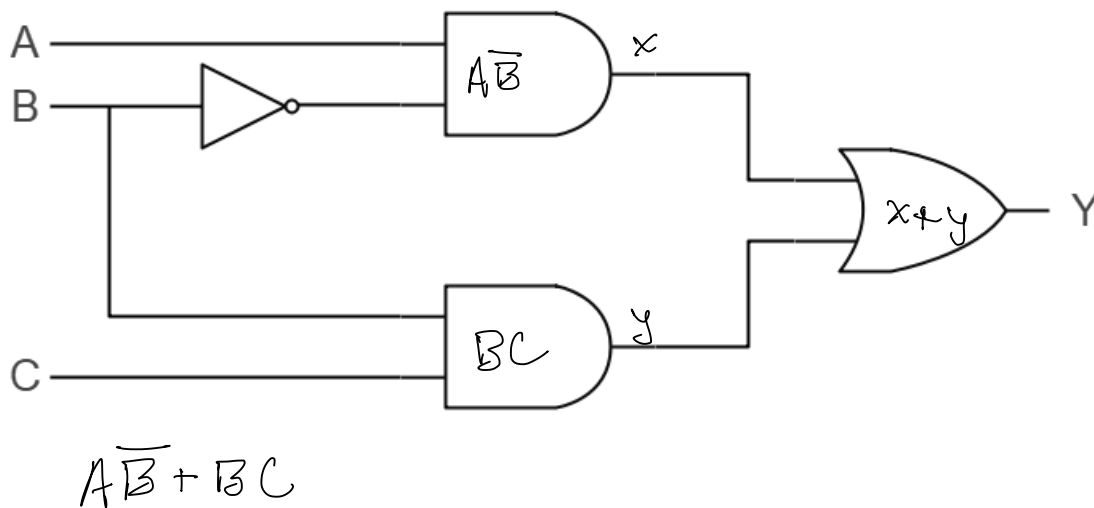- a. Write the Boolean equation for the circuit shown below. No need to simplify.



- b. Rename the inputs and outputs as follows:

A = D0

C = D1

B = Select

Y = Out

$$(D0 \cdot \overline{\text{Select}}) + (\text{Select} \cdot D1)$$

What is the name of this circuit? It is a widely used combinational circuit (see Lecture 6).

It's a 2-to-1 multiplexer